

Figure 1a shows a standard CMOS inverter. However, during manufacturing, the circuit was contaminated with a particle and the gate of the PMOS transistor got shorted to GND. The contaminated inverter circuit could be modeled as shown in Figure 1b.

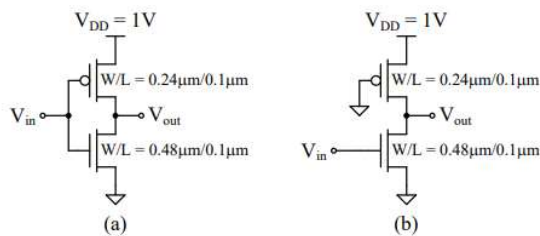


Figure 1: CMOS Inverter.

(Note: L indicates drawn channel length).

1A Find  $V_{OH}$ ,  $V_{OL}$ , and  $V_M$  for the inverters in Figures 1a and 1b.  
(Don't assume that  $V_M = V_{DD}/2$ , do some hand calculation)

1A

Assume typical value for low output voltage and high output voltage of CMOS Inverter and given that  $V_{CC} = V_{DD} = 1V$

$$V_{OH} = 1V : V_{OH} = V_{CC} \rightarrow V_{OL} = 0$$

$$V_{OL} = 0V$$

Find  $V_M$ , assume transistors are saturated.

$$\text{NMOS stronger: } \frac{k_n}{k_p} = \frac{K_n'}{K_p'} \cdot \frac{(\frac{W}{L})_n}{(\frac{W}{L})_p} : (\frac{W}{L})_n > (\frac{W}{L})_p$$

$$I_{dN} = \frac{1}{2} K_n' \left( \frac{W}{L} \right)_n (V_{GS} - V_{TH})_n^2 (1 + \lambda V_{DS})_n$$

$$(0.5)(140)(5.64)(V_M - 0.17)^2 (1 + 0.75 V_M)$$

$$394.8 [V_M^2 - 0.34 V_M + 0.0289] [1 + 0.75 V_M]$$

$$394.8 [V_M^2 - 0.34 V_M + 0.0289 + 0.75 V_M^3 - 0.255 V_M^2 + 0.021675 V_M]$$

$$394.8 [0.75 V_M^3 + 0.405 V_M^2 - 0.3183 V_M + 0.0289]$$

$$I_{dP} = \frac{1}{2} K_p' \left( \frac{W}{L} \right)_p (V_{GS} - V_{TH})_p^2 (1 + \lambda V_{DS})_p$$

$$= (0.5)(100)(2.82)(1 - V_M - 0.2)^2 (1 + 0.62(1 - V_M))$$

$$141 [0.8 - V_M]^2 [1.62 - 0.62 V_M]$$

$$.5 * 140 * 5.64 = 394.8, .5 * 100 * 2.82 = 141$$

$$I_{dP} = I_{dN} \rightarrow$$

using software

$$V_M \approx 0.40911 \text{ or complex results}$$

1B

Let input voltage be  $V_{OH} = 1V$ , then  
assume  $V_{OL} < V_{DSAT} \rightarrow$  NMOS is in Linear  
region while PMOS is saturated.

assume  $V_{OL} < V_{DSAT} \rightarrow$  NMOS is in Linear region while PMOS is saturated.

Sat Lin VSAT

$$M_n : \min(V_{gt}, V_{DS}, V_{DSAT}) = \min(V_M - V_T, V_M, 0.3)$$

$$= \min(V_M - 0.17, \underline{V_M}, 0.3)$$

$$M_p : \min(|V_{gt}|, |V_{DS}|, |V_{DSAT}|) = \min(1 - V_M - V_T, 1 - V_M, 0.4)$$

$$= \min(1 - V_M - 0.2, 1 - V_M, 0.4) = \min(\underline{0.8 - V_M}, 1 - V_M, 0.4)$$

NMOS off during  $V_{OL} \rightarrow V_{OH} = 1V, V_{OL} = 0.12V$

$$I_{dN} = K'_n \left(\frac{W}{L}\right)_n \left[ (V_{GS} - V_{TH}) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right]_n (1 + \lambda V_{DS})_n$$

$$(140)(5.64) \left[ (V_M - 0.17) 0.3 - 0.045 \right] (1 + 0.75 V_M)$$

$$I_{dP} = K'_p \left(\frac{W}{L}\right)_p \left[ (V_{GS} - V_{TH})_p V_{DS} - \frac{V_{DS}^2}{2} \right]_p (1 + \lambda V_{DS})_p$$

$$(100)(2.82) \left[ (1 - V_M - 0.2)(1 - V_M) - \frac{1}{2}(1 - V_M)^2 \right] (1 + 2(1 - V_M))$$

$$282(1 - V_M) \left[ (1 - 0.2) - \frac{1}{2}(1 - V_M) \right] (1.62 - 0.62 V_M)$$


140\*5.64=789.6


$$I_{dN} = I_{dP} \rightarrow V_M \approx -0.79, 0.578, 5.26$$

Using Software

$$\underline{V_M \approx 0.578V}$$

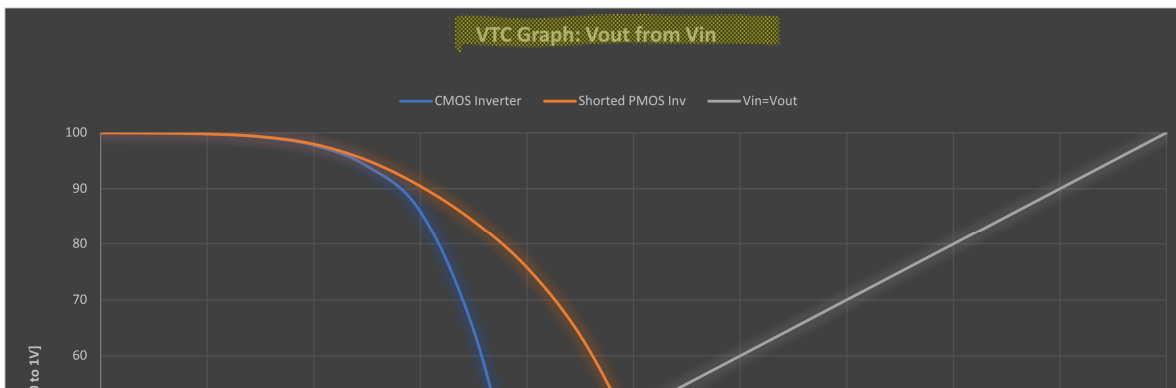For the below curve I had to scale the left side as millivolts to get the graph values to show correctly in Excel



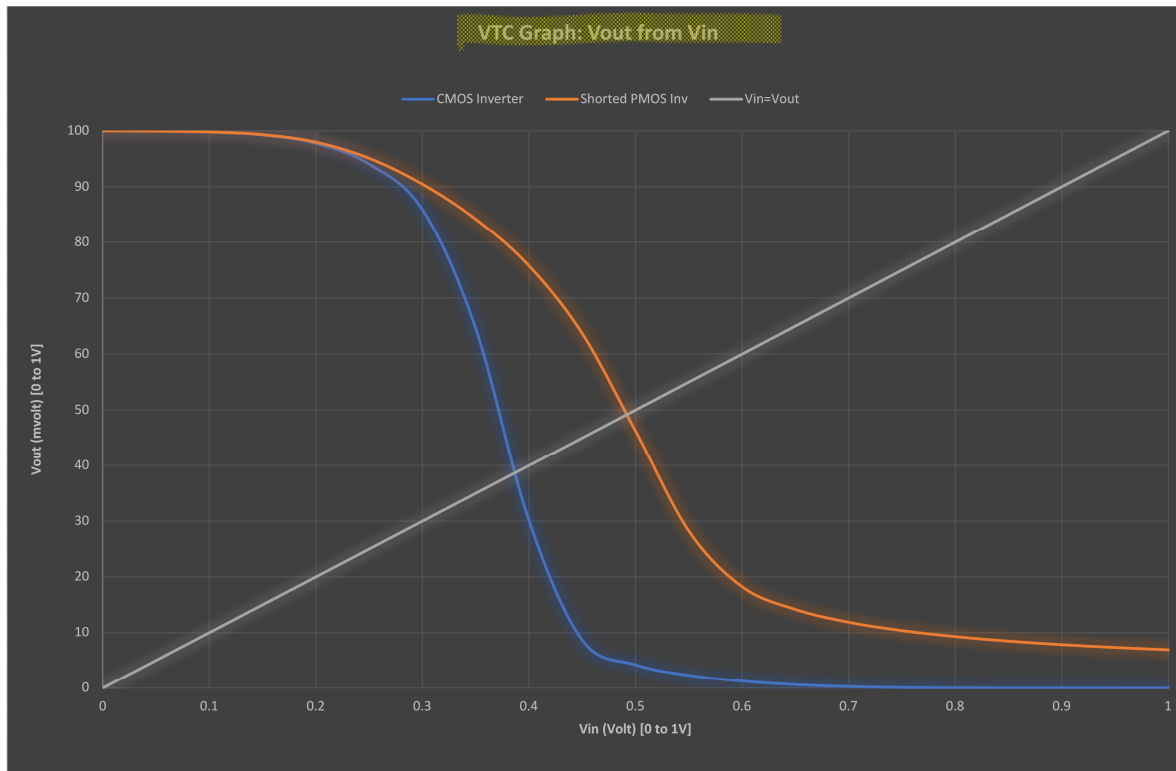

**VTC Curves:** The Maximum Low Output Voltage of the inverter is actually not zero in our PMOS shorted to ground circuit. We also see a right shift due to this transistor shorting to ground compared with our CMOS Inverter, so the drop in output voltage occurs at higher input voltages. This may indicate that the PMOS never fully shut off as we would expect both NMOS and PMOS to change states throughout the graph, but the output voltage never went completely to 0.

**Robustness:** The PMOS shorted figure is considered less robust. Consider  $NM_L$  such that  $V_{IL} - V_{OL}$  can be analyzed from either line curve such that  $NM_L < NM_H$  proving this analysis of robustness.

**Regeneration:** Both curves appear to closely represent the graphs we studied in class in both shape and a nice steepness where we would expect slopes to approximate to -1. However, it is clear upon analysis that the CMOS inverter does have a steeper dropoff for the undefined region where we expect the MOSFETs to start switching. Because of the larger gain for the first curve, there is faster regeneration there.

2)

$$\textcircled{1} I_{DSAT} = K' \left( \frac{W}{L} \right) \left( (V_{DD} - V_{TH}) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

$$\textcircled{2} R_{on-approx} = \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \frac{V_{DD}}{V_{DSAT}} \right)$$

Ron VDD	Idsat (uA)	Analytical Model (Req)	Simulation
.4	7.6	29.1	27.8
.6	26.29	10.3	9
.8	44.9	6.2	6.5

.6	26.29	10.3	9
.8	44.9	6.2	6.5
1	63.6	3.9	5

Lambda is held as a constant in these calculations but often this value can change along with changes in  $V_{gs}$ . So a better depiction of the results could be obtained from looking at different values of  $V_{gs}$  since  $V_{gs}$  is linked to the  $V_{cc}$  or  $V_{dd}$  that is typically fed into the inverter. It is likely that if we used the adjusted lambda values for each  $V_{gs}$  corresponding to it, then we may get more accurate values to  $R_{on}$  simulated.

We also note that the values for  $V_{dd}$  and possibly  $V_{gs}$  of 0.8 and 1 have a smaller percent error from the expected simulation values. Therefore, there is likely an error that arises from using our calculations for lower values of  $V_{dd}$  and  $V_{gs}$  with our formulas. It is likely that  $V_{dsat}$  is not necessarily in the saturation region this early and is giving slightly off results. This would justify why our later values in analytical model are closer to simulation values.

3l

3a

$V_{il}$	.3
$V_{ih}$	.6
$V_{ol}$	.2
$V_{oh}$	.9
NMI	.1
NMh	.3

3b

$$(i) \quad E_{H(i)} = C_L [V_{DD} - \frac{1}{2} \cdot 1^2] = 100(1 - \frac{1}{2}) = 50 \text{ fJ}$$

$$(ii) \quad E_{H(ii)} = C_L [\frac{1}{2} \cdot 1^2 - \frac{1}{2} (0.3)^2] = 50(1 - 0.09) = 45.5 \text{ fJ}$$

$$(iii) \quad E_{H(iii)} = C_L [V_{DD}(1 - 0.3) - \frac{1}{2} (1^2 - 0.3^2)] = 100 [1(0.7) - \frac{1}{2} (.91)] = 24.5 \text{ fJ}$$

i	50 fJ
ii	45.5 fJ
iii	24.5 fJ